

**U.G. 3rd Semester Examination - 2020**

**PHYSICS**

**[HONOURS]**

**Generic Elective Course (GE)**

**Course Code : PHY-H-GE-P-1**

**(Electricity and Magnetism)**

**[PRACTICAL]**

Full Marks : 20

Time : 2 Hours

*The figures in the right-hand margin indicate marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

Answer any **four** questions: 5×4=20

1. What is series resonance in an electric circuit? Draw the necessary circuit diagram. Derive an expression of resonant frequency and quality factor for the above circuit. 1+2+2
2. Write down the Thevenin's and Norton's theorems. Draw the circuit diagram of De' Sauty's bridge. 2+3
3. What is the CDR and current sensitivity of a ballistic galvanometer? Write the formula for measurement of the charge Q flowing through a ballistic galvanometer. 2+2+1

4. Draw the circuit diagram for the measurement of high resistance by the method of leakage of charge of a charge condenser. What order of resistance can be measured by this method? Can you measure this resistance by a P.O box? Explain your answer. 3+1+1
5. Write the Maximum power transfer theorem. Write the necessary formula to calculate the self inductance of a coil by Rayleigh's method. What order of resistance can be measured by a Carey-Foster bridge? 2+2+1
6. What do you understand by the term "Impedance", "Reactance" and "Power factor" of an A.C circuit? What is a parallel resonant circuit? 3+2

-----